
Computing in carbon

Neuroelectronics


- > membranes
- > ion channels
- > wiring

Simplified neuron models

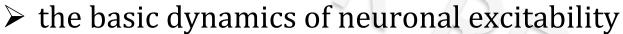


Neuronal geometry


Dendrites and dendritic computing

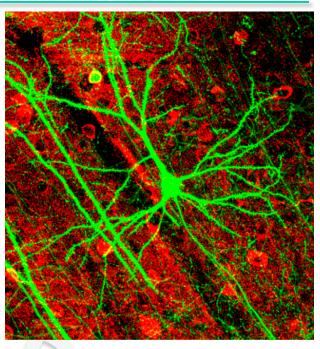

Equivalent circuit model

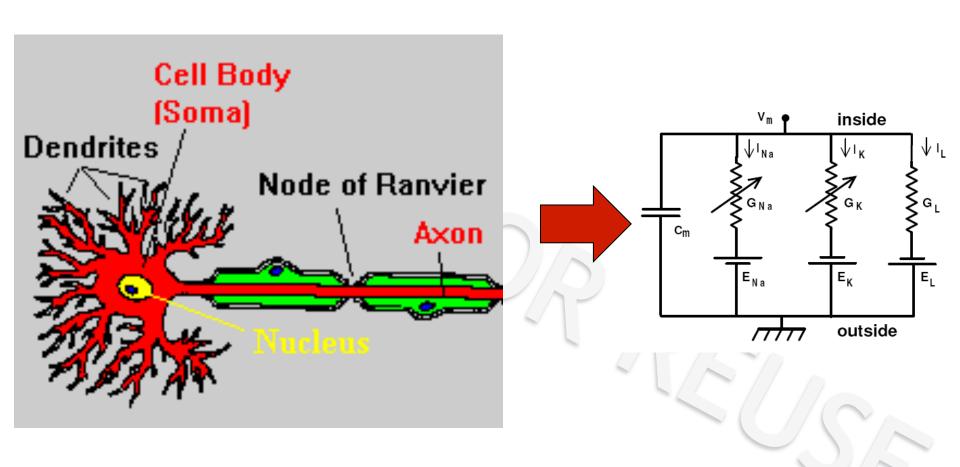

RC circuits

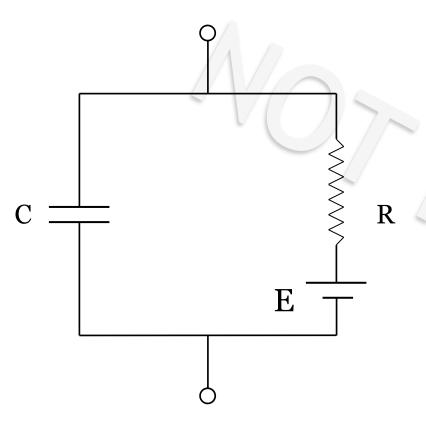


- Across a wire, the potential is the same
- The charge flowing into one element must equal the charge flowing out
- At a junction of wires, the total current is zero: Kirchhoff's law
- ➤ The potential changes by a fixed amount across a battery symbol
- ➤ The potential changes by a variable amount across a resistor symbol:


Ohm's law: V = IR or I = Vg




Membrane patch

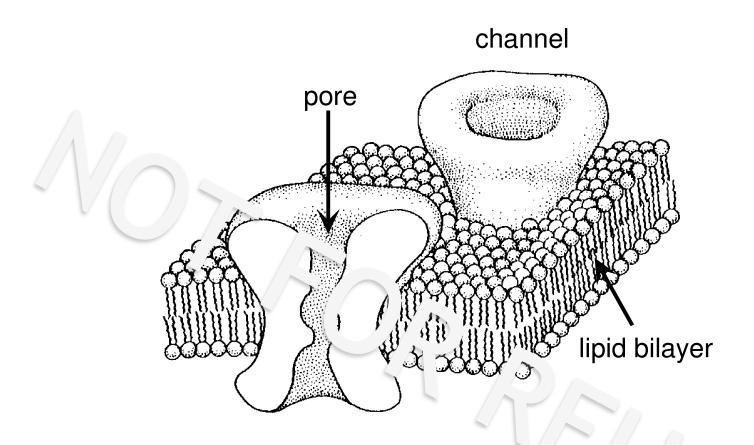

The passive membrane

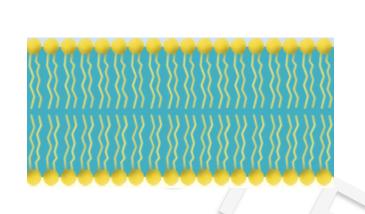

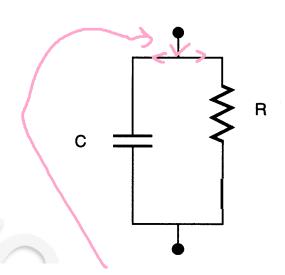

Kirchhoff:

 $I_R + I_C + I_{\text{ext}} = 0$

Ohm's law:

 $V = I_R R$

Capacitor:


$$C = Q/V$$

$$C = Q/V$$


$$I_C = C \frac{dV}{dt}$$

$$C\frac{dV}{dt} = -\frac{V}{R} + I_{\text{ext}}$$

The cell has a battery

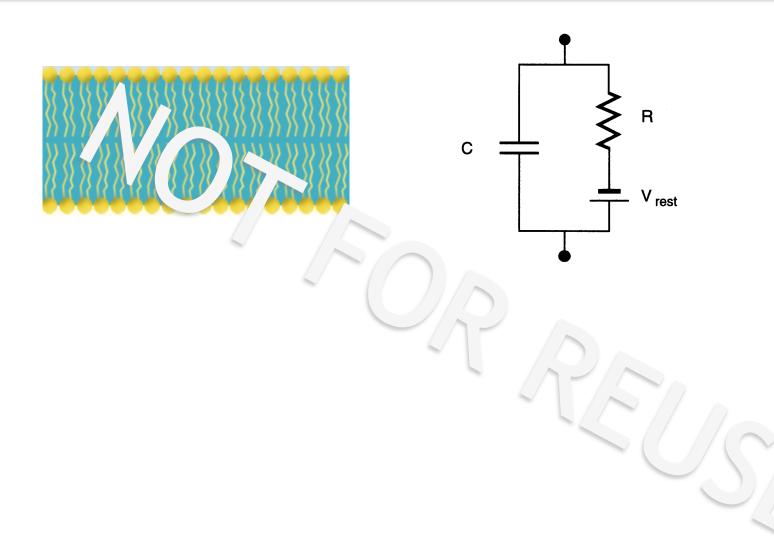


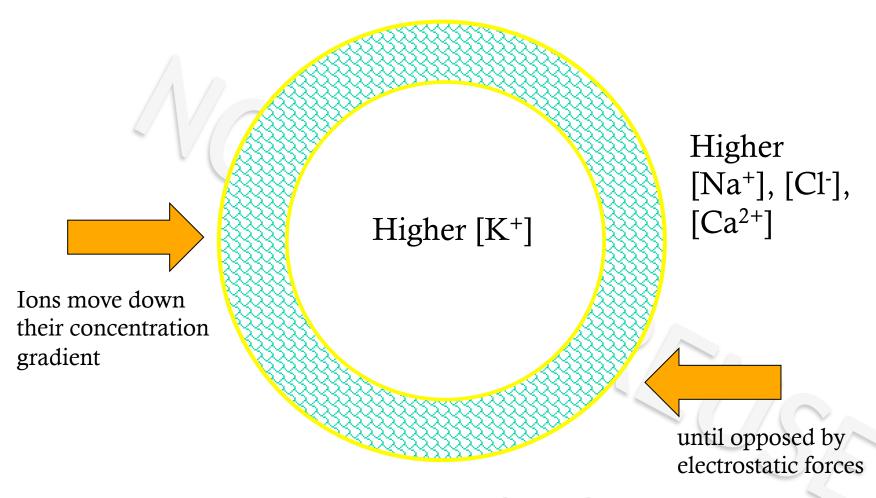
The cell's battery: the equilibrium potential



Nernst:
$$E = \frac{k_B T}{zq} \ln \frac{[\text{inside}]}{[\text{outside}]}$$


The cell has a battery

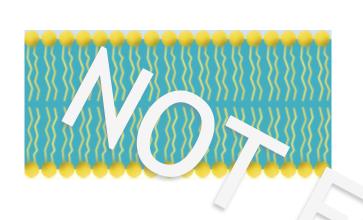

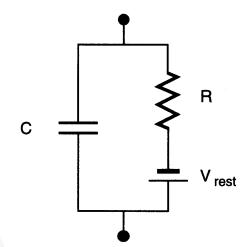

$$C\frac{dV}{dt} = -\frac{(V - V_{\text{rest}})}{R} + I_{\text{ext}}$$


How does such a membrane behave?

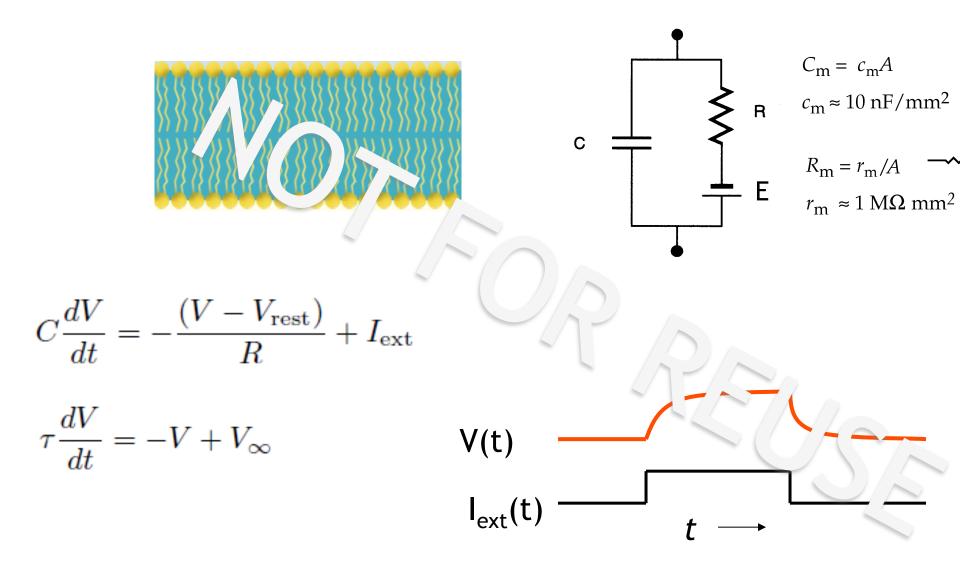

Each ion type is independent and has its own battery

Different ion channels have associated conductances.

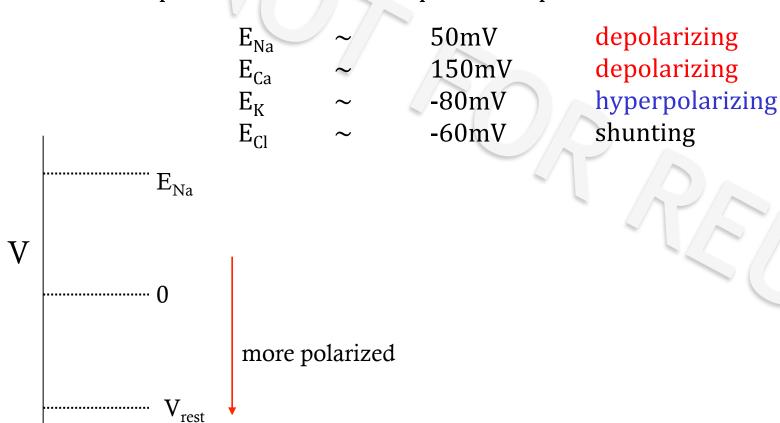A given conductance tends to move the membrane potential toward the equilibrium potential for that ion



But what makes a neuron *compute*?

